



AROR UNIVERSITY
OF ART, ARCHITECTURE,
DESIGN & HERITAGE,
SUKKUR, SINDH

Faculty of Artificial Intelligence & Multimedia Gaming

BS – Artificial Intelligence (Section A and B)

Digital Logic Design Lab

Lab # 09: Multiplexer and De-Multiplexer

Mr. Abdul Ghafoor

Submission Profile

Name:

Submission date (dd/mm/yy):

Marks obtained:

Comments:

Instructor

Lab Learning Objectives:

Upon successful completion of this experiment, the student will be able:

- Reflect on the similarities and differences between encoders and multiplexers
- Examine the function of a Multiplexer and De- Multiplexer using logic gates
-

Lab Hardware and Software Required:

<i>Platform: NI ELVIS III</i>	<ul style="list-style-type: none">✓ View User Manual: http://www.ni.com/en-us/support/model.ni-elvis-iii.html✓ View Tutorials: https://www.youtube.com/playlist?list=PLvcPIuVaUMIWm8ziaSxv0gwtshBA2dh_M
<i>Software: NI Multisim 14.0.1 Education Version or newer</i>	<ul style="list-style-type: none">✓ Install Multisim: http://www.ni.com/gate/gb/GB_ACADEMICEVALMULTISIM/US✓ View Help: http://www.ni.com/multisim/technical-resources/

Background Theory:

Multiplexers

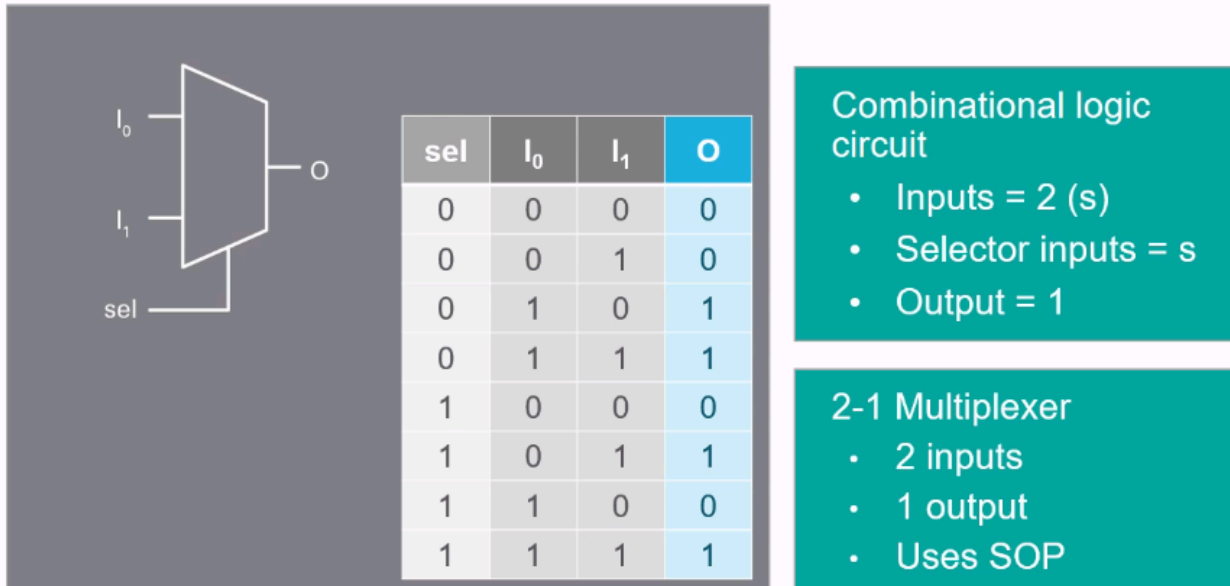


Figure 1-1 Video. View the video here: https://youtu.be/khmQ-LT_Cxg



Video Summary

- Multiplexers are combinational logic circuits
- Clock multiplexing is used for operating the same logic function at different clock rates from different sources
- Demultiplexers are combinational logic circuits that have the opposite function of a multiplexer

Multiplexers

The *multiplexer*, abbreviated *MUX*, is a combinational logic circuit which has multiple data inputs, one or more select inputs and one output.

- It passes the data on one of the inputs, depending on the selection signals, to the output
- With the help of this logic circuit, multiple signals can share the same data output
- Multiplexers have $2s$ inputs and s selector lines, which determine which of the inputs to output.
- Multiplexers are one of the most widely used combinational circuits, their application areas include:
 - Data routing
 - Operation sequencing

- Parallel-to-serial conversion
- Waveform generation

The simplest circuit is the 2-to-1 multiplexer, with the graphical symbol presented in the leftmost figure. Its functionality is described by the joining truth table. The multiplexer below is only 1-bit wide since bit line is connected to a single output bit line.

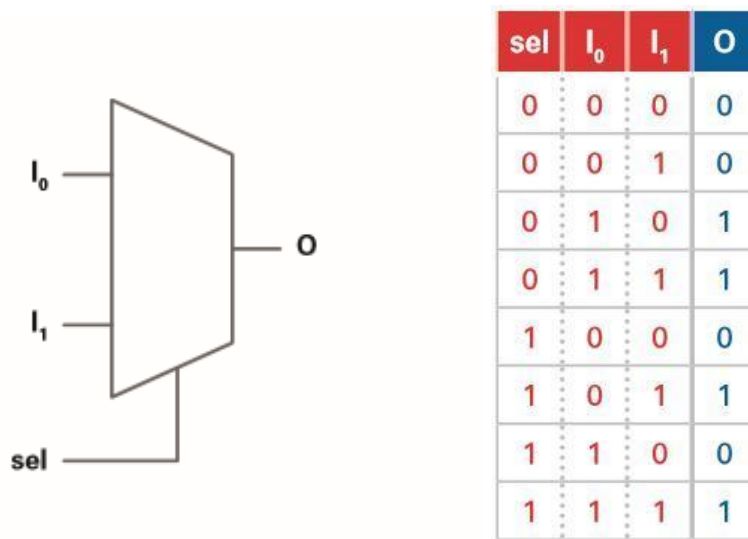


Figure 1-2 Image of 2-to-1 multiplexer (left) and truth table (right)

The truth table can be simplified to the following truth table for a better understanding of the circuit's operation:

sel	O
0	I_0
1	I_1

Figure 1-3 Simplified truth table

Using the sum-of-products Boolean function gives the following combinational logic circuit:

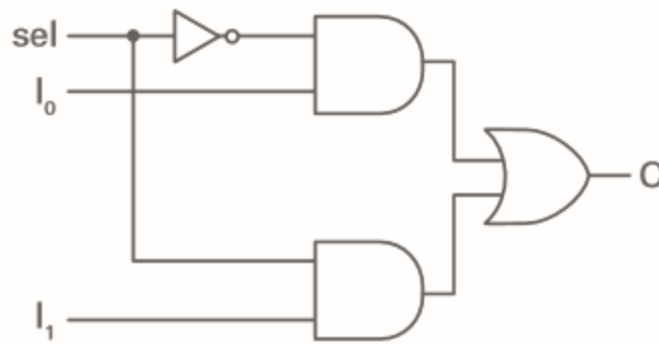


Figure 1-4 Combinational logic circuit

Clock multiplexing is a technique used for operating the same logic function at different clock rates, from different sources (inputs).

- The logic circuits are switched by the select signal often while the circuit is running
- This process of switching isn't very safe and can result in a glitch that occurs when one signal is going down as the other is going up.
- Clock safe switches can be implemented to eliminate glitches.

Demultiplexers

Demultiplexers (DEMUX) have the opposite function of a multiplexer

- It places the value of a single data input on several data outputs depending on a selection signal
- Usually demultiplexers have s select inputs and 2^s outputs
- Since demultiplexers take one input and connect it to many outputs, some of their uses are for communication (two-way communication usually includes both multiplexers and demultiplexers) and for serial to parallel converters
- The graphical symbol for a 1-to-4 demultiplexer is shown below (left) as well as the corresponding 1-to-4 DEMUX truth table (centre) and the CLC (right)

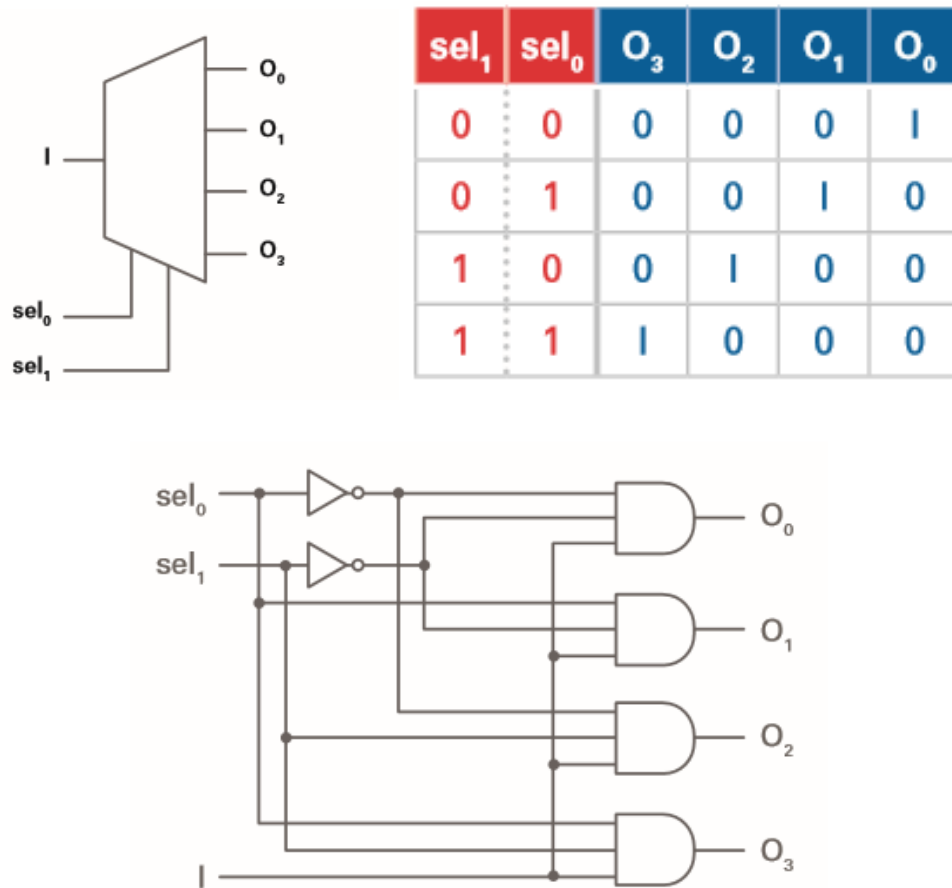


Figure 1-5 Demultiplexer (top left), truth table (top center) and CLC (bottom)

1-1 Write the sum-of-products Boolean functions for the 2-to-1 Multiplexer:

1-2 Write the sum-of-products Boolean functions for the 1-to-4 Demultiplexer:

1-3 What is the function of the Selector (Sel) in Multiplexers and Demultiplexers?

- Use a Venn diagram to show the similarities and differences between Encoders and Multiplexers. Add the file, picture, or a screenshot of the Venn diagram to your completed lab.

Lab Activities:

4-to-1 MUX

Using the following truth table (right) to describe the behavior of a 4-to-1 MUX (left), design and implement the corresponding circuit in multisim.

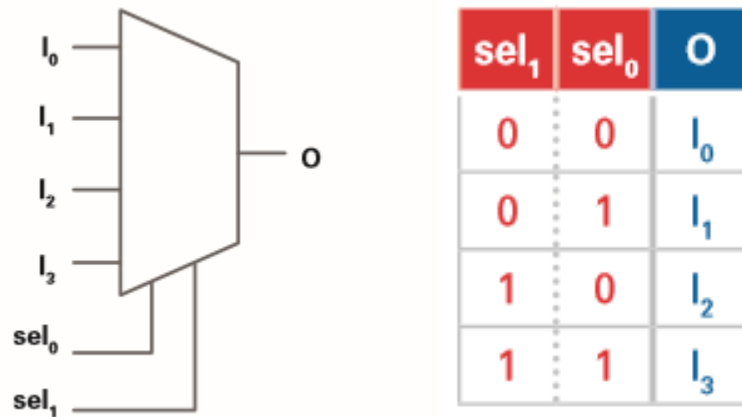


Figure 1-8 Image of 4-to-1 MUX (left) and truth table (right)

1-to-4 Demultiplexer

In simulation build and run the following 1-to-4 demultiplexer

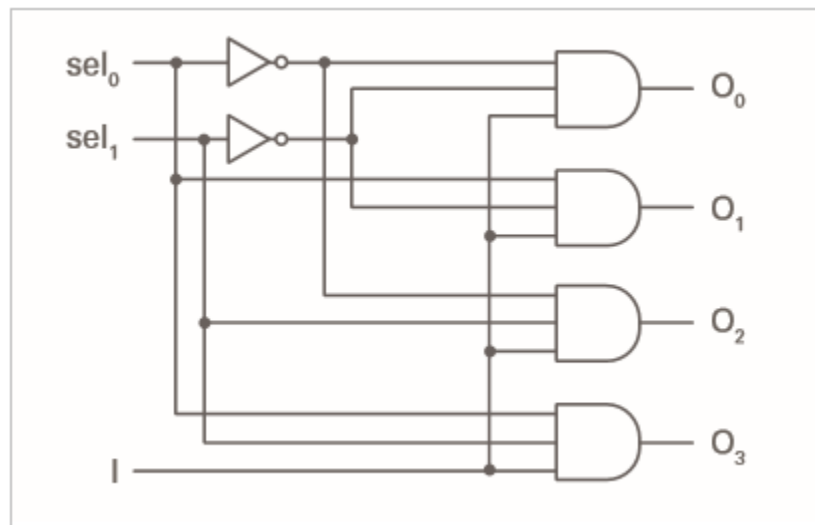


Figure 1-9 Image of 1-to-4 demultiplexer

Lab Exercise:

- Implement 4 to 1 multiplexer circuit on **NI-ELVIS II** using 74HC153/74LS153
- Implement 1 to 4 de-multiplexer circuit on **NI-ELVIS II** using 74HC155/74LS155
- Implement 8 to 1 multiplexer by cascading two 74HC153/74LS153

Conclusion:

1-4 In an everyday application, when would a multiplexer be useful?

1-5 In an everyday application, when would a demultiplexer be useful?

1-6 How many outputs does a multiplexer have?

- A. 1
- B. 2
- C. 3
- D. 2^n

1-7 Why can the truth table of a 2-to-1 multiplexer be simplified depending on whether the selector is set to 0 or 1?

- A. There is only one output
- B. Some of the outputs of the original truth table are don't care conditions
- C. The line that is selected to be inputted will be the only one affecting the output
- D. None of the above

1-8 The 1-to-4 demultiplexer has how many selectors?

- A. 4
- B. 3
- C. 2
- D. None of the above

1-9 What is the difference between the logic circuit of a 2-to-4 decoder and a 1-to-4 demultiplexer?

- A. They use a different combination of logic gates
- B. They have a different number of outputs
- C. They have different inputs
- D. All of the above