



AROR UNIVERSITY
OF ART, ARCHITECTURE,
DESIGN & HERITAGE,
SUKKUR, SINDH

Faculty of Artificial Intelligence & Multimedia Gaming

BS – Artificial Intelligence (Section A)

Digital Logic Design Lab

Lab # 05:

Mr. Abdul Ghafoor

Submission Profile

Name:

Submission date (dd/mm/yy):

Marks obtained:

Comments:

Instructor

Task 01: Sum of Product (SOP)

A. Construct a digital circuits of the given Boolean expression in Multisim, which is presented in a non-standard Sum of Product (SOP) format.

1. $AB' + B' + A'C + C$
2. $AB'C' + CB' + A'C'$
3. $A' + B' + AC'$
4. $AB' + AC' + ABC'$

Add snapshot of circuits of above expressions

1	
2	
3	

4	
---	--

- B. Convert the non-standard SOP expression from A into the standard SOP format and then build its digital circuit representation as a standard SOP Boolean expression in Multisim.

Note: use the pen paper to convert the non-standard SOP to Standard SOP, add the snapshot of the solutions below

1	
2	

3	
4	

Add snapshot of circuits of above standard SOP expressions

1	
2	
3	
4	

--	--

C. Fill the following truth table for output of the both standard SOP and standard SOP circuits.

$AB+B'+AC+C$

A	B	C	Output of Non-Standard SOP	Output Standard SOP
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$A'BC'+AB'+AC'$

A	B	C	Output of Non-Standard SOP	Output Standard SOP
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$A+B+C$

A	B	C	Output of Non-Standard SOP	Output Standard SOP
0	0	0		
0	0	1		
0	1	0		
0	1	1		

1	0	0		
1	0	1		
1	1	0		
1	1	1		

AB+AC+BC'

A	B	C	Output of Non-Standard SOP	Output Standard SOP
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Task 02: Product of Sum (POS)

A. Construct a digital circuits of the given Boolean expression in Multisim, which is presented in a non-standard Product of Sum (POS) format.

1. $(A'+B') \cdot (A'+B'+C) \cdot (A+C)$
2. $(B'+C) \cdot (B'+C) \cdot (A+B'+C')$
3. $(A' \cdot (A'+B))$

Add snapshot of circuits of above POS expressions

1	
---	--

2	
3	

- B. Convert the non-standard POS expression from A into the standard POS format and then build its digital circuit representation as a standard POS Boolean expression in Multisim.

Note: use the pen paper to convert the non-standard POS to Standard POS, add the snapshot of the solutions below

1	
---	--

2	
3	

Add snapshot of circuits of above standard POS expressions

1	
2	
3	

- C. Fill the following truth table for output of the both standard POS and standard POS circuits.

$(A+B) \cdot (A'+C) \cdot (A+B+C)$

A	B	C	Output of Non-Standard POS	Output Standard POS
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$(B+C) \cdot (B' + C) \cdot (A' + B' + C')$

A	B	C	Output of Non-Standard POS	Output Standard POS
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$(A) \cdot (A' + B')$

A	B	C	Output of Non-Standard POS	Output Standard POS
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		